

Experiment 3: The research of Thevenin theorem


1. Purpose

- Validate Thevenin theorem;
- Master the methods to measure the equivalent parameters of linear two-terminal active network.
- Study the conditions of the maximum output power in the linear two-terminal active network.

2. Principal and Illustration

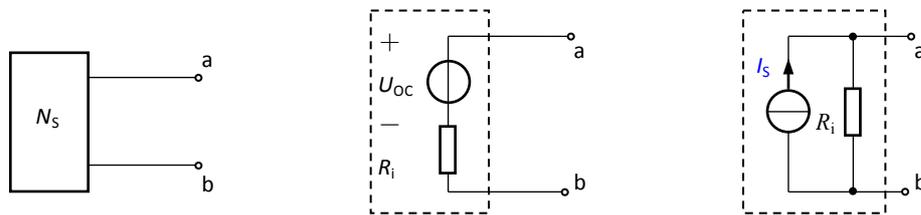A. Linear two-terminal active network and its equivalent circuit.

In any linear two-terminal active network N_S , as shown in Figure 3-3-1(a), if only studying the external circuit of the network, we can regard the network as Thevenin equivalent circuit of resistance and voltage source in series, as shown in Figure 3-3-1(b), or Norton equivalent circuit of resistance and current source in parallel, as shown in Figure 3-3-1(c).



(a) Linear two-terminal active network (b)Thevenin equivalent circuit (c)Norton equivalent circuit

Thevenin theorem: Any linear active two-terminal network always can be replaced by voltage and current source for the external circuit. The voltage U_S of voltage source is equal to open circuit voltage U_{OC} of the two-terminal active network and its resistance R_i is equal to the equivalent resistance R_{eq} after all independent sources set to be zero.

B. Methods to measure the equivalent parameters of linear two-terminal active networks

(1) Open circuit voltage method and short circuit current method

Use a voltmeter to measure open circuit voltage U_{OC} between the output terminals of the network directly when the output terminals are open connected. Then, use an ammeter to measure the current I_{SC} of the network when the output terminals are short connected. The equivalent resistance of the

two-terminal network can be estimated by:

$$R_{eq} = \frac{U_{OC}}{I_{SC}} \quad (3-3-1)$$

(2) *Voltage-current method*

Use a voltmeter and an ammeter to measure the external characteristic of the two-terminal active network, as shown in Figure 3-3-2. Utilize the external characteristic curve to calculate slope $\tan(\varphi)$. The equivalent resistance of the two-terminal network can be estimated by:

$$R_{eq} = \tan \varphi = \frac{\Delta U}{\Delta I} = \frac{U_{OC}}{I_{SC}} \quad (3-3-2)$$

If the internal resistance of two-terminal network is very small, it's not suitable to measure short circuit current. We can use voltage-current method in this case, to measure the open circuit voltage U_{OC} , and the output voltage U_N when the current of the two-terminal active network is fixed to I_N . The equivalent resistance of the two-terminal network can be estimated by:

$$R_{eq} = \frac{U_{OC} - U_N}{I_N} \quad (3-3-3)$$

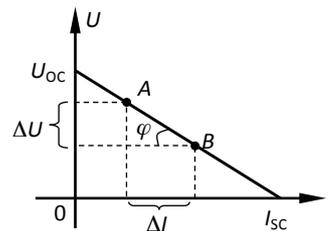


Figure 3-3-2 voltage-current characteristic of active two-terminal network

(3) *Half voltage method*

As shown in Figure 3-3-3, when load voltage is half of the open circuit voltage of the measured network, the resistance of load resistor is equal to the equivalent internal resistance R_{eq} of the two-terminal active network.

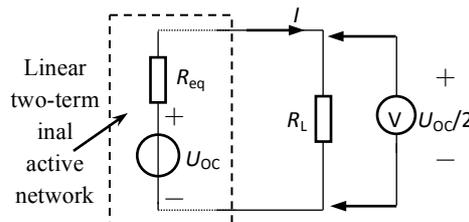


Figure 3-3-3 Use half voltage method to measure R_{eq} circuit

(4) *Zero Method*

If the two-terminal active network has a high internal resistance, using a voltmeter to directly measure it may cause a rather big error. In this case, we can use Zero method to eliminate the effect of the internal resistance of the Voltmeter.

The principal of zero method: comparing the two-terminal active network with a voltage-stabilized source of low internal resistance, when the output voltage of the voltage-stabilized source is equal to the open circuit voltage of the two-terminal active network, the voltmeter shows “0”, as shown in figure 3-3-4. Then, open the electric circuit and measure the output voltage of the voltage-stabilized source, which is equal to the open circuit voltage of the measured active two-terminal network.

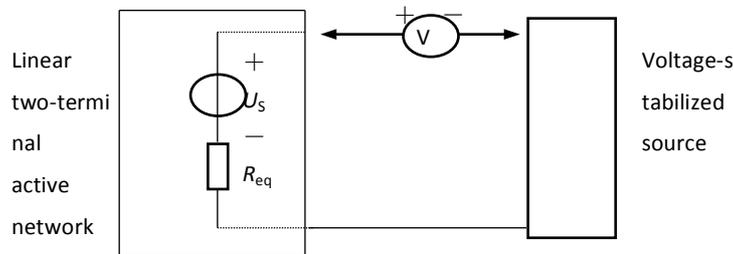


Figure 3-3-4 Use zero method to measure U_s

3. Contents and Steps

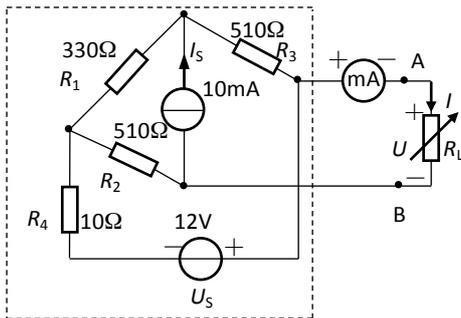


Figure 3-3-5 the external characteristic circuit of the two-terminal active network

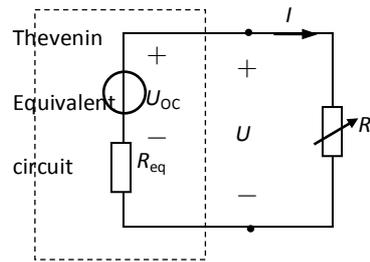


Figure 3-3-6 Thevenin equivalent circuit

A. Use open circuit voltage method and short circuit current method to measure U_{oc} and R_{eq} of the two-terminal active network

As show in Figure 3-3-5, the voltage-stabilized source U_s and constant-current source I_s are connected into the linear two-terminal active network. Open the circuit at load R_L to get the two terminals A and B, then, use

D. The study of the conditions of maximum power transfer.

Based on the data you record in Step “C”, calculate the power absorbed by R_L and record these values into Table 3-3-4.

Table 3-3-4. The measured data for studying the maximum power transfer conditions in Thevenin equivalent circuit.

| | | | | | | | | | | | | | |
|---------------|---|-----|-----|-----|-----|----------|-----|-----|-----|----|----|----|----------|
| $R_L(\Omega)$ | 0 | 100 | 400 | 450 | 500 | R_{eq} | 550 | 600 | 800 | 1k | 2k | 5k | ∞ |
| $P(W)$ | | | | | | | | | | | | | |

4. Questions

- What is the condition of measuring I_{sc} in the short circuit experiment to obtain the Thevenin equivalent circuit?
- Can we directly short connect the circuit in the experiment?
- Summarize the methods to measure the open circuit voltage and equivalent internal resistance of the two-terminal active network, and compare their advantage and disadvantage.

5. Writing your reports

- Based on the data you recorded in Step “B” and Step “C”, plot the respective voltage-current characteristics curves and validate the Thevenin theorem.
- Based on the data you recorded in Step “D”, plot the curve of power P versus R_L as R_L changes continually, $P = f(R_L)$. Validate whether the maximum power transfer condition is correct or not. In other words, when $R_L = R_{eq}$, whether the power absorbed by the load R_L is the largest.