

Problem # 1

What is the phase sequence of each of the following sets of voltages?

a) $v_a = 208 \cos(\omega t + 27^\circ) \text{ V},$

$v_b = 208 \cos(\omega t + 147^\circ) \text{ V},$

$v_c = 208 \cos(\omega t - 93^\circ) \text{ V}.$


b) $v_a = 4160 \cos(\omega t - 18^\circ) \text{ V},$

$v_b = 4160 \cos(\omega t - 138^\circ) \text{ V},$

$v_c = 4160 \cos(\omega t + 102^\circ) \text{ V}.$

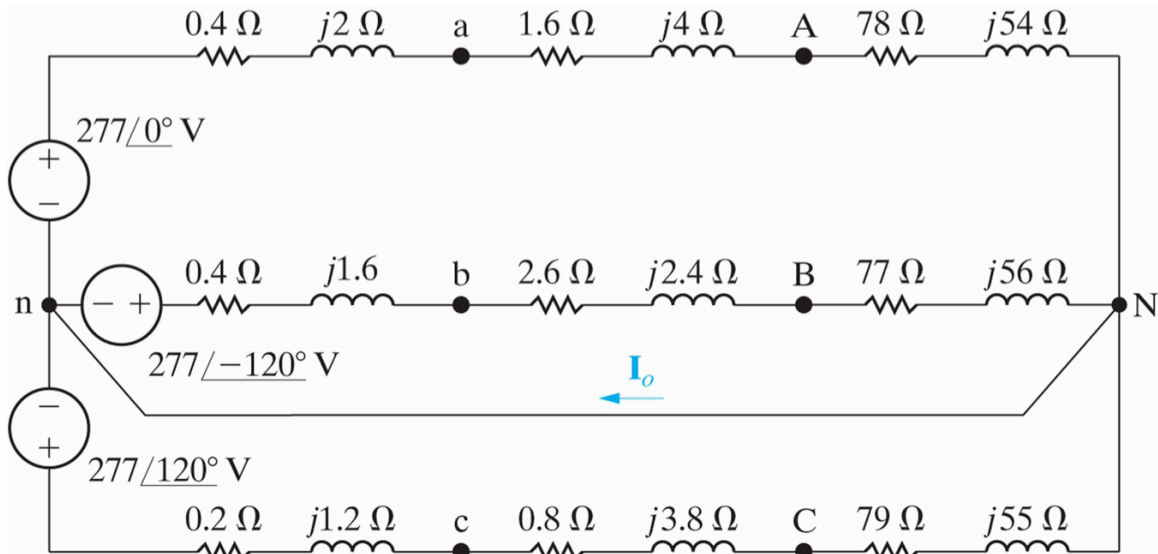Problem #2


Find the rms value of I_o in the unbalanced three-phase circuit.



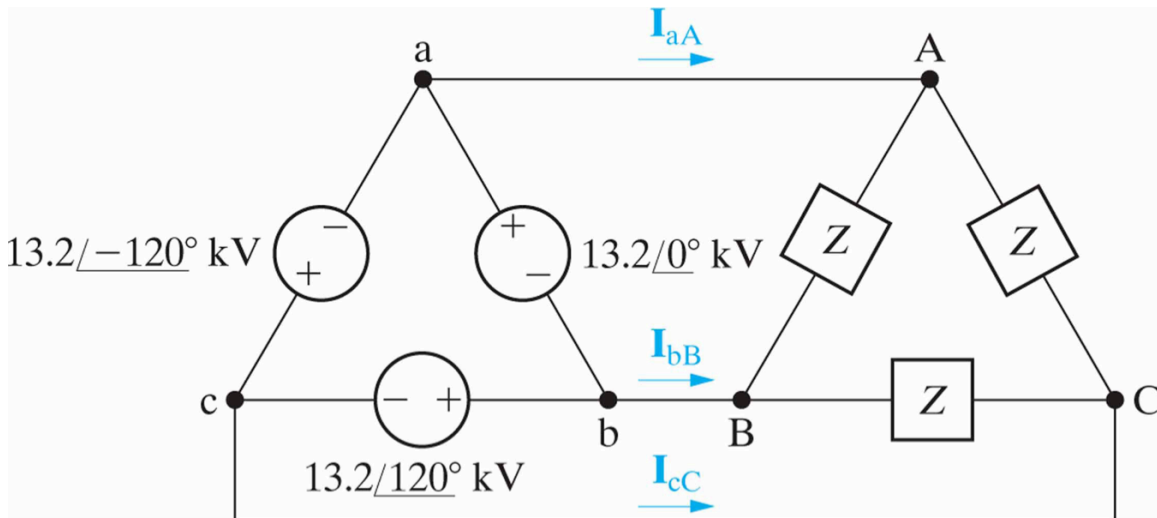Problem #3

The impedance Z in the balanced three-phase circuit is $100 - j75 \Omega$. Find

- I_{AB} , I_{BC} , and I_{CA} ,
- I_{aA} , I_{bB} , and I_{cC} ,
- I_{ba} , I_{cb} , and I_{ac} .



Problem #4

A three-phase line has an impedance of $0.1 + j0.8 \Omega/\phi$. The line feeds two balanced three-phase loads connected in parallel. The first load is absorbing a total of 630 kW and absorbing 840 kVAR magnetizing vars. The second load is Y-connected and has an impedance of $15.36 - j4.48 \Omega/\phi$. The line-to-neutral voltage at the load end of the line is 4000 V. What is the magnitude of the line voltage at the source end of the line?

Problem #5

- a) Calculate the reading of each wattmeter in the circuit when $Z = 13.44 + j46.08\Omega$.
- b) Check that the sum of the two wattmeter readings equals the total power delivered to the load.
- c) Check that $\sqrt{3}(W_1 - W_2)$ equals the total magnetizing vars delivered to the load.