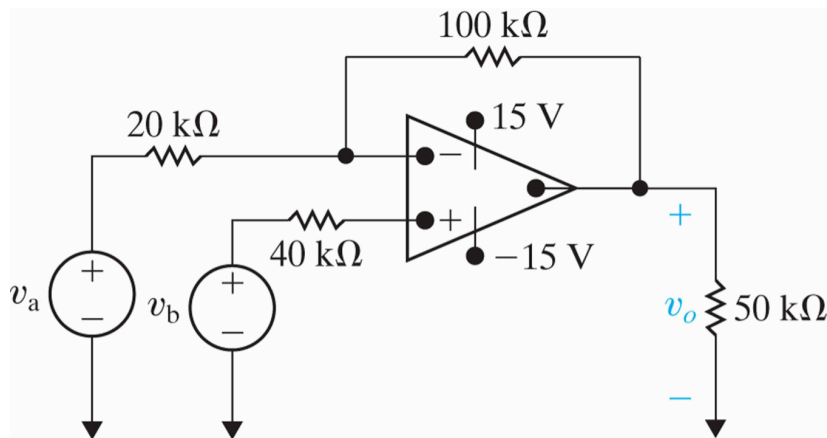


Problem # 1

The op amp in the circuit is ideal.


- a) Calculate v_o if $v_a = 4\text{V}$ and $v_b = 0\text{V}$.
- b) Calculate v_o if $v_a = 2\text{V}$ and $v_b = 0\text{V}$.
- c) Calculate v_o if $v_a = 2\text{V}$ and $v_b = 1\text{V}$.
- d) Calculate v_o if $v_a = 1\text{V}$ and $v_b = 2\text{V}$.
- e) Calculate v_o if $v_a = 1.5\text{V}$ and $v_b = 4\text{V}$.

If $v_b = 1.6\text{ V}$, specify the range of v_a such that the amplifier does not saturate.



Problem #2

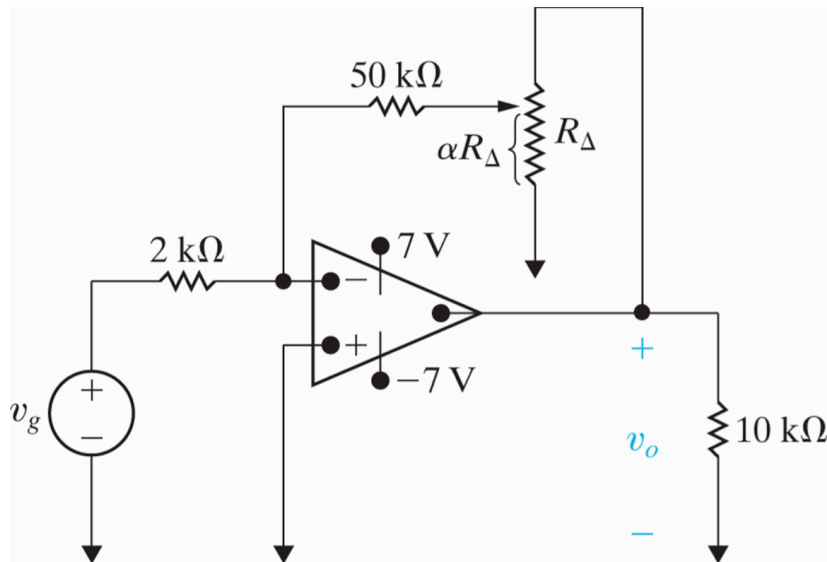- a) The op amp in the circuit shown is ideal. The adjustable resistor R_{Δ} has a maximum value of $100 \text{ k}\Omega$, and α is restricted to the range of $0.2 < \alpha < 1$. Calculate the range of v_o if $v_g = 40 \text{ mV}$.
- b) If α is not restricted, at what value of α will the op amp saturate?



Problem #3

Design an inverting-summing amplifier so that


$$v_o = -(3 v_a + 5 v_b + 4 v_c + 2 v_d).$$

Start by choosing a feedback resistor (R_f) from Appendix H. Then choose single resistors from Appendix H or construct resistor networks from resistors in Appendix H to satisfy the design values for R_a , R_b , R_c , and R_d . Draw your final circuit diagram.

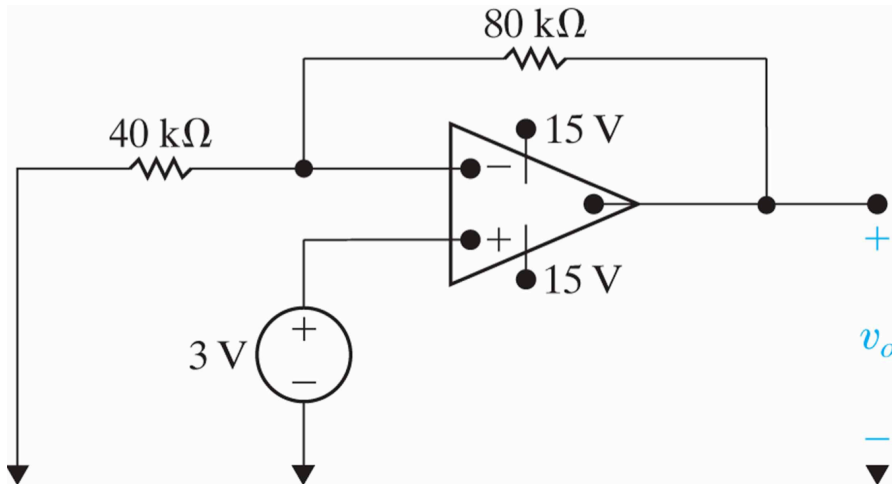Problem #4

The op amp in the circuit is ideal.

- What op amp circuit configuration is this?
- Calculate v_o .



Problem #5

The op amp in the circuit is ideal. What value of R_f will give the equation $v_o = 5 - 4v_a$ for this circuit?

