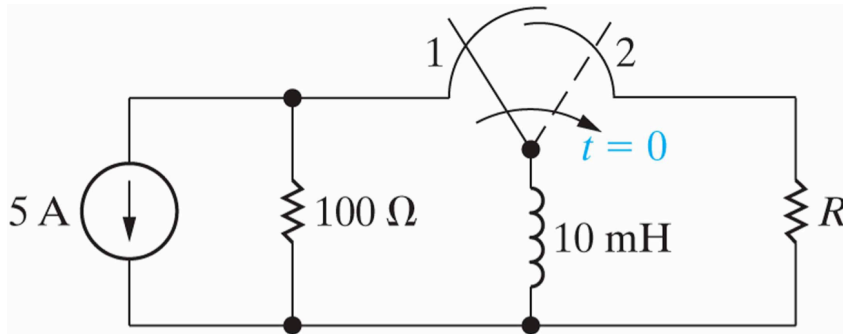


## Problem #1

The switch in the circuit has been in position 1 for a long time. At  $t = 0$ , the switch moves instantaneously to position 2. Find the value of  $R$  so that 10% of the initial energy stored in the 10 mH inductor is dissipated in  $R$  in  $10 \mu\text{s}$ .



## Problem #2


In the circuit, the voltage and current expressions are

$$v = 72e^{-500t} \text{ V}, \quad t \geq 0;$$

$$i = 9e^{-500t} \text{ mA}, \quad t \geq 0^+.$$

Find

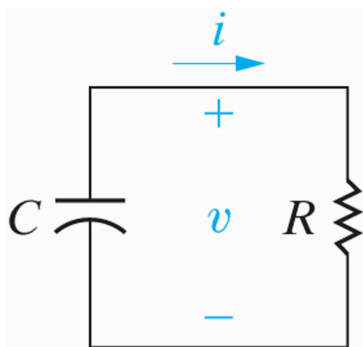- $R$ .
- $C$ .
- $\tau$  (in milliseconds).
- The initial energy stored in the capacitor.
- How many microseconds it takes to dissipate 68% of the initial energy stored in the capacitor.




## Problem #3

The current and voltage at the terminals of the inductor in the circuit are

- Specify the numerical values of  $V_s$ ,  $I$ ,  $I_0$ , and  $L$ .
- How many milliseconds after the switch has been closed does the energy stored in the inductor reach 9 J?

$$i(t) = (4 + 4e^{-40t}) \text{ A}, \quad t \geq 0;$$
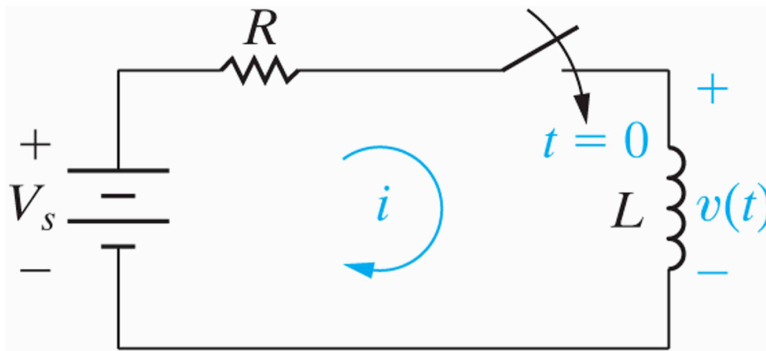
$$v(t) = -80e^{-40t} \text{ V}, \quad t \geq 0^+.$$




## Problem #4

There is no energy stored in the circuit at the time the switch is closed.


- Find  $i(t)$  for  $t \geq 0$ .
- Find  $v_1(t)$  for  $t \geq 0^+$ .
- Find  $v_2(t)$  for  $t \geq 0$ .

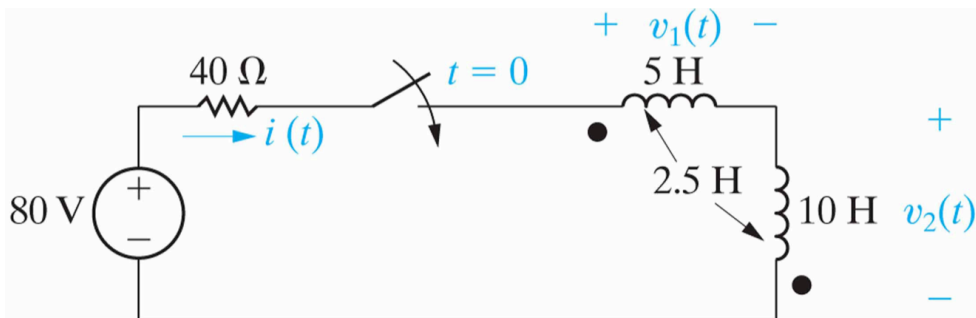Do your answers make sense in terms of known circuit behavior?


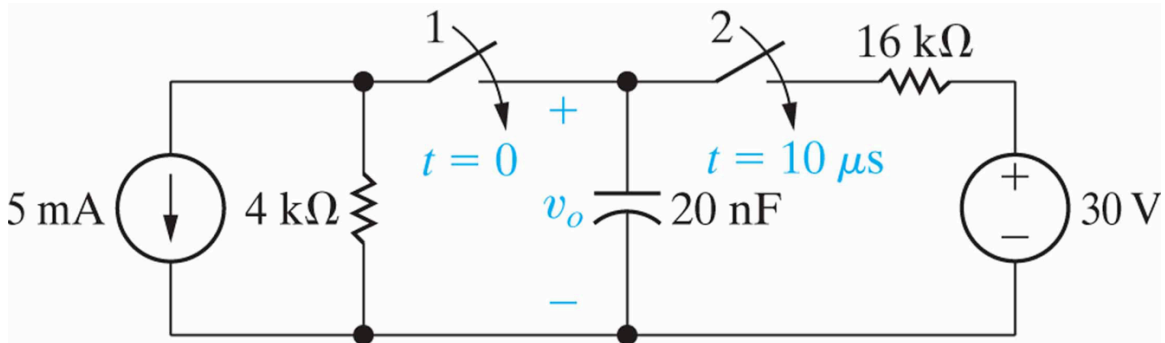
## Problem #5

There is no energy stored in the capacitor in the circuit when switch 1 closes at  $t = 0$ . Ten microseconds later, switch 2 closes. Find  $v_o(t)$  for  $t \geq 0$ .



## Problem #6

The capacitor in the circuit shown is charged to 20 V at the time the switch is closed. If the capacitor ruptures when its terminal voltage equals or exceeds 20 kV, how long does it take to rupture the capacitor?

