

## Problem # 1

The resistance, inductance, and capacitance in a parallel  $RLC$  circuit are  $2000\ \Omega$ ,  $250\ \text{mH}$ , and  $10\ \text{nF}$ , respectively.

- Calculate the roots of the characteristic equation that describe the voltage response of the circuit.
- Will the response be over-, under-, or critically damped?
- What value of  $R$  will yield a damped frequency of  $12\ \text{krad/s}$ ?
- What are the roots of the characteristic equation for the value of  $R$  found in (c)?
- What value of  $R$  will result in a critically damped response?


## Problem #2

The voltage response for the circuit is known to be

$$v(t) = D_1 t e^{-500t} + D_2 e^{-500t}, \quad t \geq 0.$$

The initial current in the inductor ( $I_0$ ) is  $-10\ \text{mA}$ , and the initial voltage on the capacitor ( $V_0$ ) is  $8\ \text{V}$ . The inductor has an inductance of  $4\ \text{H}$ .

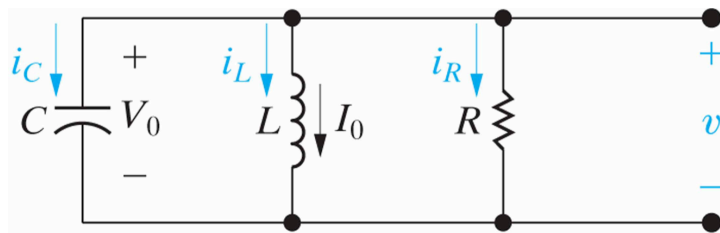- Find the values of  $R$ ,  $C$ ,  $D_1$  and  $D_2$ .
- Find  $i_o(t)$  for  $t \geq 0^+$ .




## Problem #3

The switch in the circuit has been open a long time before closing at  $t=0$ . Find

a)  $v_o(t)$  for  $t \geq 0^+$ ,

b)  $i_L(t)$  for  $t \geq 0$ .

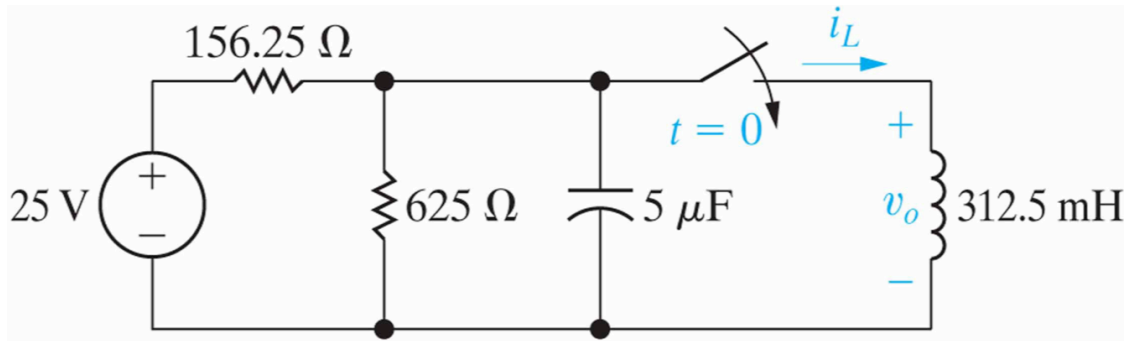


## Problem #4

The switch in the circuit has been closed for a long time. The switch opens at  $t = 0$ . Find

a)  $i_o(t)$  for  $t \geq 0$ ,

b)  $v_o(t)$  for  $t \geq 0$ .

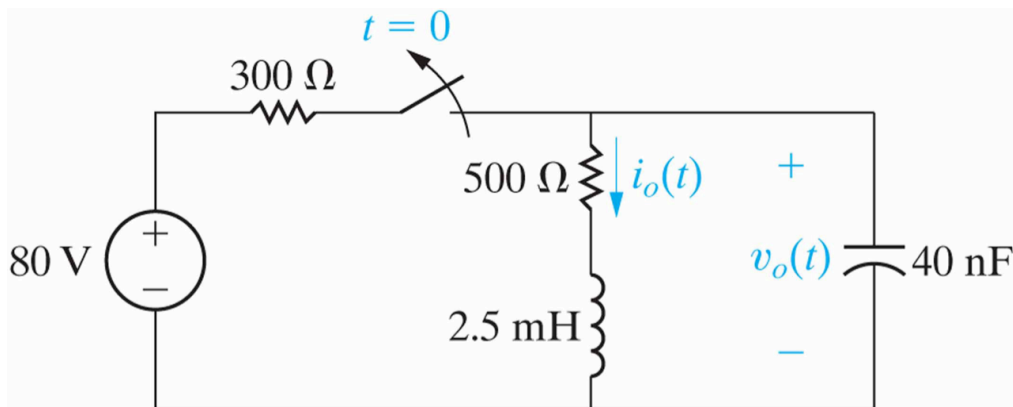

## Problem #5

The voltage signal is applied to the cascaded integrating amplifiers. There is no energy stored in the capacitors at the instant the signal is applied.

- Derive the numerical expressions for  $v_o(t)$  and  $v_{o1}(t)$  for the time intervals  $0 \leq t \leq 0.5$  s and  $0.5$  s  $\leq t \leq t_{sat}$ .
- Compute the value of  $t_{sat}$ .

