

Problem # 1

At $t = -2$ ms, a sinusoidal voltage is known to be zero and going positive. The voltage is next zero at $t = 8$ ms. It is also known that the voltage is 80.9 V at $t = 0$.

- What is the frequency of v in hertz?
- What is the expression for v ?

Problem #2

Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:


- $y = 50 \cos(500t + 60^\circ) + 100 \cos(500t - 30^\circ)$,
- $y = 200 \cos(377t + 50^\circ) - 100 \sin(377t + 150^\circ)$
- $y = 80 \cos(100t + 30^\circ) - 100 \sin(100t - 135^\circ) + 50 \cos(100t - 90^\circ)$, and
- $y = 250 \cos \omega t + 250 \cos(\omega t + 120^\circ) + 250 \cos(\omega t - 120^\circ)$.

Problem #3

- Show that, at a given frequency ω , the circuits in the Figure (a) and (b) will have the same impedance between the terminals a, b if


$$R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2}, \quad L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2}.$$

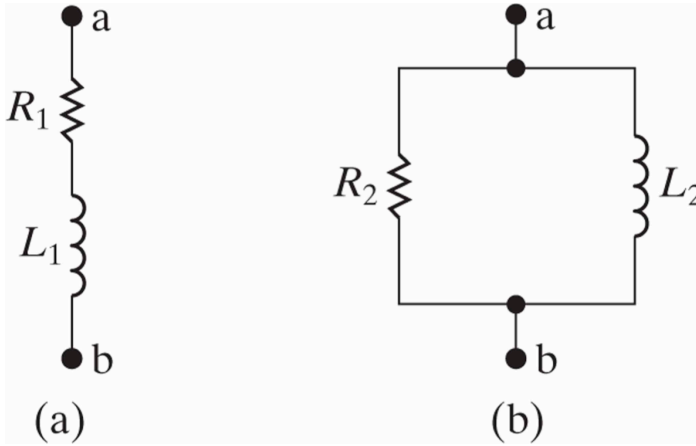- Find the values of resistance and inductance that when connected in series will have the same impedance at 4 krad/s as that of a 5 k Ω resistor connected in parallel with a 1.25 H inductor.



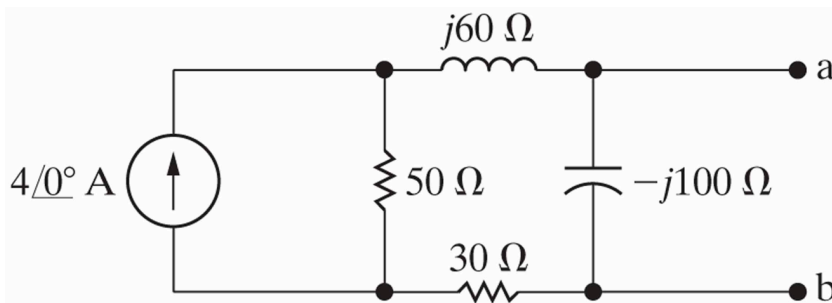Problem #4

Use source transformations to find the Norton equivalent circuit with respect to the terminals a, b for the circuit.




Problem #5

Use the node-voltage method to find the steady-state expression for $v_o(t)$ in the circuit if

$$v_{g1} = 20 \cos(2000t - 36.87^\circ) \text{ V},$$
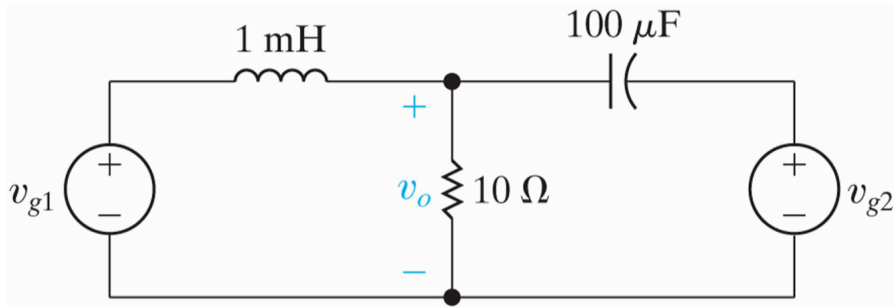
$$v_{g2} = 50 \sin(2000t - 16.26^\circ) \text{ V}.$$



Problem #6

Use the mesh-current method to find the steady-state expression for $i_o(t)$ in the circuit if

$$v_a = 60 \cos 40,000t \text{ V,}$$

$$v_b = 90 \sin (40,000t + 180^\circ) \text{ V.}$$

